

1.41

(a) $I_{D1} = I_{D2} = 1 \text{ mA}$

(i) $V_{D1} = V_{D2} = (0.026) \ln \left(\frac{10^{-3}}{10^{-13}} \right) = 0.599 \text{ V}$

(ii) $V_{D1} = (0.026) \ln \left(\frac{10^{-3}}{5 \times 10^{-14}} \right) = 0.617 \text{ V}$

$$V_{D2} = (0.026) \ln \left(\frac{10^{-3}}{5 \times 10^{-13}} \right) = 0.557 \text{ V}$$

(b) $V_{D1} = V_{D2}$

(i) $I_{D1} = I_{D2} = \frac{I_i}{2} = 0.5 \text{ mA}$

$$V_{D1} = V_{D2} = (0.026) \ln \left(\frac{0.5 \times 10^{-3}}{10^{-13}} \right) = 0.581 \text{ V}$$

(ii) $\frac{I_{D1}}{I_{D2}} = \frac{I_{S1}}{I_{S2}} = \frac{5 \times 10^{-14}}{5 \times 10^{-13}} = 0.10$

So $I_{D1} = 0.10 I_{D2}$

$$I_{D1} + I_{D2} = 1.1 I_{D2} = 1 \text{ mA}$$

So $I_{D2} = 0.909 \text{ mA}$, $I_{D1} = 0.0909 \text{ mA}$

Now

$$V_{D1} = (0.026) \ln \left(\frac{0.0909 \times 10^{-3}}{5 \times 10^{-14}} \right) = 0.554 \text{ V}$$

$$V_{D2} = (0.026) \ln \left(\frac{0.909 \times 10^{-3}}{5 \times 10^{-13}} \right) = 0.554 \text{ V}$$

1.42

(a) $I_{D3} = (6 \times 10^{-14}) \exp \left(\frac{0.635}{0.026} \right) \Rightarrow 2.426 \text{ mA}$


$$I_R = \frac{0.635}{1} = 0.635 \text{ mA}$$

$$I_{D1} = I_{D2} = 2.426 + 0.635 = 3.061 \text{ mA}$$

$$V_{D1} = V_{D2} = (0.026) \ln \left(\frac{3.061 \times 10^{-3}}{6 \times 10^{-14}} \right) = 0.641 \text{ V}$$

$$V_I = 2(0.641) + 0.635 = 1.917 \text{ V}$$

1.44

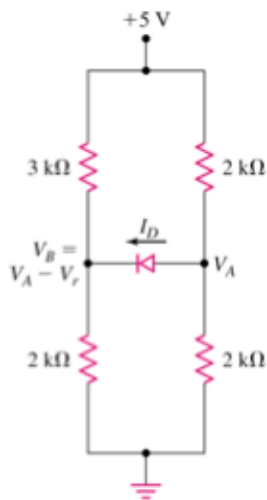

At node V_A :

$$(1) \quad \frac{5 - V_A}{2} = I_D + \frac{V_A}{2}$$

At node $V_B = V_A - V_r$:

$$(2) \quad \frac{5 - (V_A - V_r)}{2} + I_D = \frac{(V_A - V_r)}{2}$$

$$\text{So } \frac{5 - (V_A - V_r)}{3} + \left[\frac{5 - V_A}{2} - \frac{V_A}{2} \right] = \frac{V_A - V_r}{2}$$

Multiply by 6:

$$10 - 2(V_A - V_r) + 15 - 6V_A = 3(V_A - V_r)$$

$$25 + 2V_r + 3V_r = 11V_A$$

If the diode is assumed ON (conducting),

$$V_D = V_r = V_A - V_B = 0 \text{ V}$$

$$V_A = \frac{25 \text{ V}}{11} = 2.273 \text{ V}$$

$$I_D = \frac{5 \text{ V} - V_A}{2 \text{ k}\Omega} - \frac{V_A}{2 \text{ k}\Omega} = 2.5 \text{ mA} - \frac{2.273 \text{ V}}{1 \text{ k}\Omega} = 227 \text{ }\mu\text{A}$$

Since $I_D > 0 \text{ A}$, the diode is ON, as assumed.

Comment: A more efficient solution approach involves connecting the appropriate Thevenin equivalent circuit (voltage source and resistance) to each side of the diode. This results in a single-loop circuit that can be analyzed to determine the diode's voltage and current.

1.47


$$(a) (i) \quad I = \frac{5 - 0.7}{20} = 0.215 \text{ mA}, \quad V_O = 0.7 \text{ V}$$

$$(b) (i) \quad I = \frac{5 - 0.7 - (-5)}{40} = 0.2325 \text{ mA}, \quad V_O = (0.2325)(20) - 5 = -0.35 \text{ V}$$

$$(c) (i) \quad I = \frac{2 - 0.7 - (-8)}{25} = 0.372 \text{ mA}, \quad V_O = 2 - (0.372)(5) = 0.14 \text{ V}$$

$$(d) (i) \quad I = 0, \quad V_O = -5 \text{ V}$$

1.53

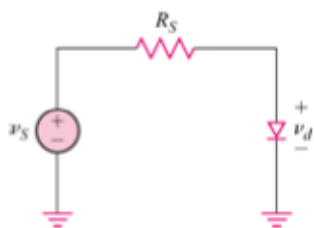

a. diode resistance $r_d = V_T/I$

$$v_d = \left(\frac{r_d}{r_d + R_s} \right) v_s = \left(\frac{V_T/I}{\frac{V_T}{I} + R_s} \right) v_s$$

$$v_d = \left(\frac{V_T}{V_T + IR_s} \right) v_s = v_o$$

b. $R_s = 260 \Omega$

$$I = 1 \text{ mA}, \quad \frac{v_o}{v_s} = \left(\frac{V_T}{V_T + IR_s} \right) = \frac{0.026}{0.026 + (1)(0.26)} \Rightarrow \frac{v_o}{v_s} = 0.0909$$

$$I = 0.1 \text{ mA}, \quad \frac{v_o}{v_s} = \frac{0.026}{0.026 + (0.1)(0.26)} \Rightarrow \frac{v_o}{v_s} = 0.50$$

$$I = 0.01 \text{ mA}, \quad \frac{v_o}{v_s} = \frac{0.026}{0.026 + (0.01)(0.26)} \Rightarrow \frac{v_o}{v_s} = 0.909$$

1.58

$$(a) \quad I_Z = \frac{10 - 6.8}{0.5} = 6.4 \text{ mA}$$

$$P = I_Z V_Z = (6.4)(6.8) = 43.5 \text{ mW}$$

$$(b) \quad I_Z = (0.1)(6.4) = 0.64 \text{ mA}$$

$$I_L = 6.4 - 0.64 = 5.76 \text{ mA}$$

$$I_L = \frac{V_Z}{R_L} \Rightarrow R_L = \frac{V_Z}{I_Z} = \frac{6.8}{5.76} = 1.18 \text{ k}\Omega$$

2.3

$$(a) \quad v_s = 120\sqrt{2}\left(\frac{1}{10}\right) = 16.97 \text{ V (peak)}$$

$$v_o(\text{peak}) = 16.27 \text{ V}$$

$$(b) \quad i_D(\text{peak}) = \frac{16.27}{2} = 8.14 \text{ mA}$$

$$(c) \quad v_o = 16.97 \sin \omega t - 0.7$$

$$\sin(\omega t)_1 = \frac{0.7}{16.97} = 0.04125 \Rightarrow (\omega t)_1 = 2.364^\circ$$

$$(\omega t)_2 = 180 - 2.364 = 177.64^\circ$$

$$\% = \left(\frac{177.64 - 2.364}{360} \right) \times 100\% = 48.7\%$$

(d)

$$\begin{aligned} v_o(\text{avg}) &= \frac{1}{2\pi} \int_{0.01313\pi}^{0.9869\pi} [16.97 \sin x - 0.7] dx \\ &= \frac{1}{2\pi} \left[(-16.97) \cos x \Big|_{0.01313\pi}^{0.9869\pi} - 0.7x \Big|_{0.01313\pi}^{0.9869\pi} \right] \\ &= \frac{1}{2\pi} [(-16.97)(-0.99915 - 0.99915) - 0.7(0.9738\pi)] \end{aligned}$$

$$v_o(\text{avg}) = 5.06 \text{ V}$$

$$(e) \quad i_D(\text{avg}) = \frac{v_o(\text{avg})}{2} = \frac{5.06}{2} = 2.53 \text{ mA}$$

2.6

$$(a) \quad v_s(\text{peak}) = 12 + 0.7 = 12.7 \text{ V}$$

$$\frac{N_1}{N_2} = \frac{120\sqrt{2}}{12.7} = 13.4$$

$$(b) \quad R = \frac{12}{0.2} = 60 \Omega$$

$$C = \frac{V_M}{2fRV_r} = \frac{12}{2(60)(60)(0.25)} \Rightarrow 6667 \mu\text{F}$$

$$(c) \quad PIV = 2v_s(\text{max}) - V_r = 2(12.7) - 0.7 = 24.7 \text{ V}$$

2.8

(a)

$$v_s(\text{max}) = 12 + 2(0.7) = 13.4 \text{ V}$$

$$v_s(\text{rms}) = \frac{13.4}{\sqrt{2}} \Rightarrow \underline{v_s(\text{rms}) = 9.48 \text{ V}}$$

(b)

$$V_r = \frac{V_M}{2f R_C} \Rightarrow C = \frac{V_M}{2f V_r R}$$

$$C = \frac{12}{2(60)(0.3)(150)} \Rightarrow \underline{C = 2222 \mu\text{F}}$$

(c)

$$i_d, \text{ peak} = \frac{V_M}{R} \left[1 + \pi \sqrt{\frac{2V_M}{V_r}} \right]$$

$$= \frac{12}{150} \left[1 + \pi \sqrt{\frac{2(12)}{0.3}} \right]$$

$$\underline{i_d, \text{ peak} = 2.33 \text{ A}}$$

2.16

$$(a) \quad v_s = 9 + 2(0.8) = 10.6 \text{ V}$$

$$\frac{N_1}{N_2} = \frac{120\sqrt{2}}{10.6} = 16$$

$$(b) \quad R = \frac{V_O}{I_L} = \frac{(9 - 0.1)V}{100 \text{ mA}} = 89 \Omega$$

$$C = \frac{V_M}{2fRV_r} = \frac{9}{2(60)(89)(0.2)} \Rightarrow 4.21 \text{ mF}$$

$$(c) \quad i_D(\text{peak}) = \frac{V_M}{R} \left(1 + \pi \sqrt{\frac{2V_M}{V_r}} \right) = \frac{9}{89} \left(1 + \pi \sqrt{\frac{2(9)}{0.2}} \right) = 3.11 \text{ A}$$

$$(a) \quad i_D(\text{avg}) = \frac{1}{\pi} \sqrt{\frac{2V_r}{V_M}} \cdot \frac{V_M}{R} \left(1 + \frac{\pi}{2} \sqrt{\frac{2V_M}{V_r}} \right) = \frac{1}{\pi} \sqrt{\frac{2(0.2)}{9}} \left(\frac{9}{89} \right) \left(1 + \frac{\pi}{2} \sqrt{\frac{2(9)}{0.2}} \right)$$

$$i_D(\text{avg}) = 0.108 \text{ A}$$

$$(c) \quad \text{PIV} = v_s(\text{max}) - V_r = 10.6 - 0.8 = 9.8 \text{ V}$$